
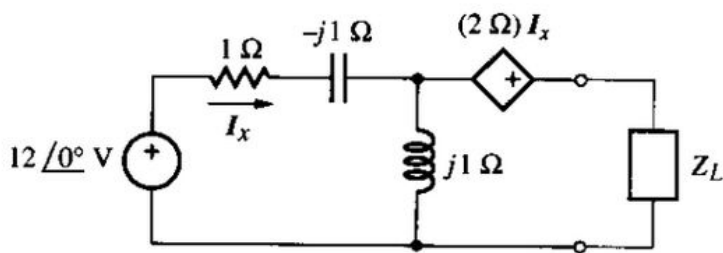


12.12 In the circuit of Figure P12.12 find the maximum average power that can be transferred to Z_L as well as Z_L itself.

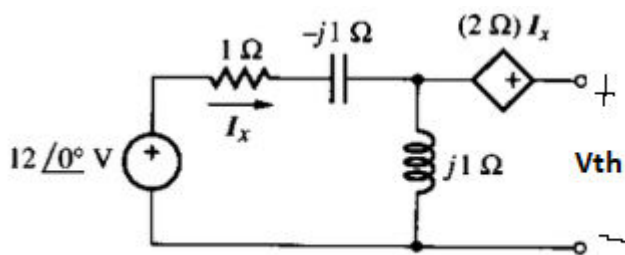12.13 Repeat Problem 12.12 for the circuit of Figure P12.13.



hallando voltaje de tyhevenin



Definimos las impedancias del circuito, sabemos que en la fuente dependiente de corriente no vamos a tener corriente

```
clc, clear ,close all
format short g
```

```
vf = 12;
```

```
z1 = 1;
z2 = -j;
z3 = j;
z4 = 2;
```

```
zeq = z1+z2+z3
```

```
zeq =
    1
```

```
Ix = 12/zeq
```

```
Ix =
    12
```

conociendo la corriente Ix podemos saber la tension en la fuente dependiente

```
v1 = Ix*z1
```

$$v1 = 12$$

$$v2 = I_x \cdot z2$$

$$v2 = 0 - 12i$$

$$v3 = I_x \cdot z3$$

$$v3 = 0 + 12i$$

$$v4 = z4 \cdot I_x$$


$$v4 = 24$$

LkT

$$V_{th} = v4 + v3$$

$$V_{th} = 24 + 12i$$

Corriente de norton

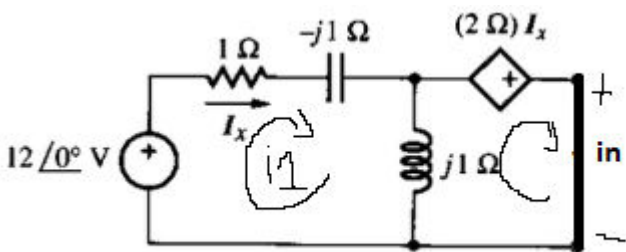

```
syms i1 i2
```

$$ec1 = \text{simplify}(v_f + (z1 \cdot i1) + (z2 \cdot i1) + z3 \cdot (i1 - i2) == 0)$$

$$ec1 = i_1 + 12 = i_2 i$$

$$ec2 = \text{simplify}(-z3 \cdot (i2 - i1) - z4 \cdot i2 == 0)$$

$$ec2 = i_1 i = i_2 (2 + i)$$

$$m = \begin{bmatrix} (-z1 - z2 - z3) & z3 \\ -z3 & (z3 - z4) \end{bmatrix};$$

$$n = [v_f; 0];$$

$$h = m \backslash n$$

$$h = 2 \times 1 \text{ complex}$$

$$\begin{matrix} -18 & - & 6i \\ -6 & + & 6i \end{matrix}$$

$$I_n = h(2)$$

$$I_n = -6 + 6i$$

Ahora quetenos la tension thevenin y corriente de norton, puedo encontrar la z thevenin

$$z_{th} = V_{th}/I_n$$

$$z_{th} = -1 - 3i$$

luego sabemos que **la impedancia de carga** es igual a la conjugada de zth

$$z_l = \text{conj}(z_{th}) \text{ %[ohms]}$$

$$z_l = -1 + 3i$$

calculamos la **potencia maxima promedio**

$$p_{max} = (\text{abs}(V_{th})^2)/(8*\text{real}(z_{th})) \text{ %[W]}$$

$$p_{max} = -90$$