

12.3 (a) Find S , P , and pf for the circuit of Figure P12.3. Is pf leading or lagging? (b) Repeat, but with the capacitance removed from the circuit. Comment on your results.

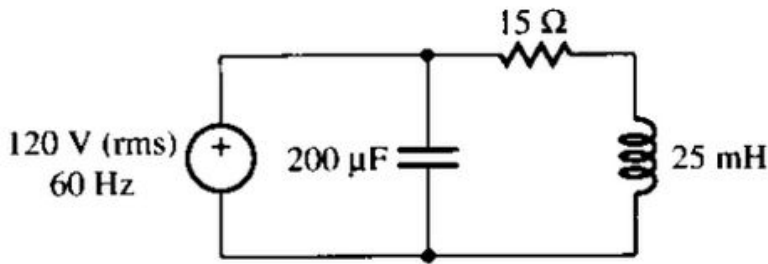


Figure P12.3

```
clc, clear, close all
format short g

vf = 120; %[V]
f = 60; %[Hz]
w = 2*pi*f;
c = 200e-6; %[F]
l = 25e-3; %[H]
r = 15; %[ohms]
gr = 180/pi; %factor de conversion de rads a grados

zc = 1/(j*w*c);
zl = j*w*l;

zeq = 1/((1/(zc))+(1/(zl+r)));
z_eq = [abs(zeq) angle(zeq)*gr] %carga capacitiva

z_eq = 1x2
    15.175    -43.505
```

Con la impedancia equivalente podemos calcular la corriente rms entregada por la fuente:

```
i_f = vf/zeq;
i_fasor = [abs(i_f) angle(i_f)*gr] %[A]

i_fasor = 1x2
    7.9079    43.505
```

con tensiones y corrientes hallamos la potencia aparente, el factor de potencia y la potencia activa:

```
S = abs(vf)*abs(i_f) %[VA]

S =
    948.95
```


```
fp = cos(angle(i_f)) %en adelanto
```

```
fp =  
    0.72531
```

```
P = S*fp %potencia activa consumida
```

```
P =  
    688.28
```

lo verificamos en el simulador:

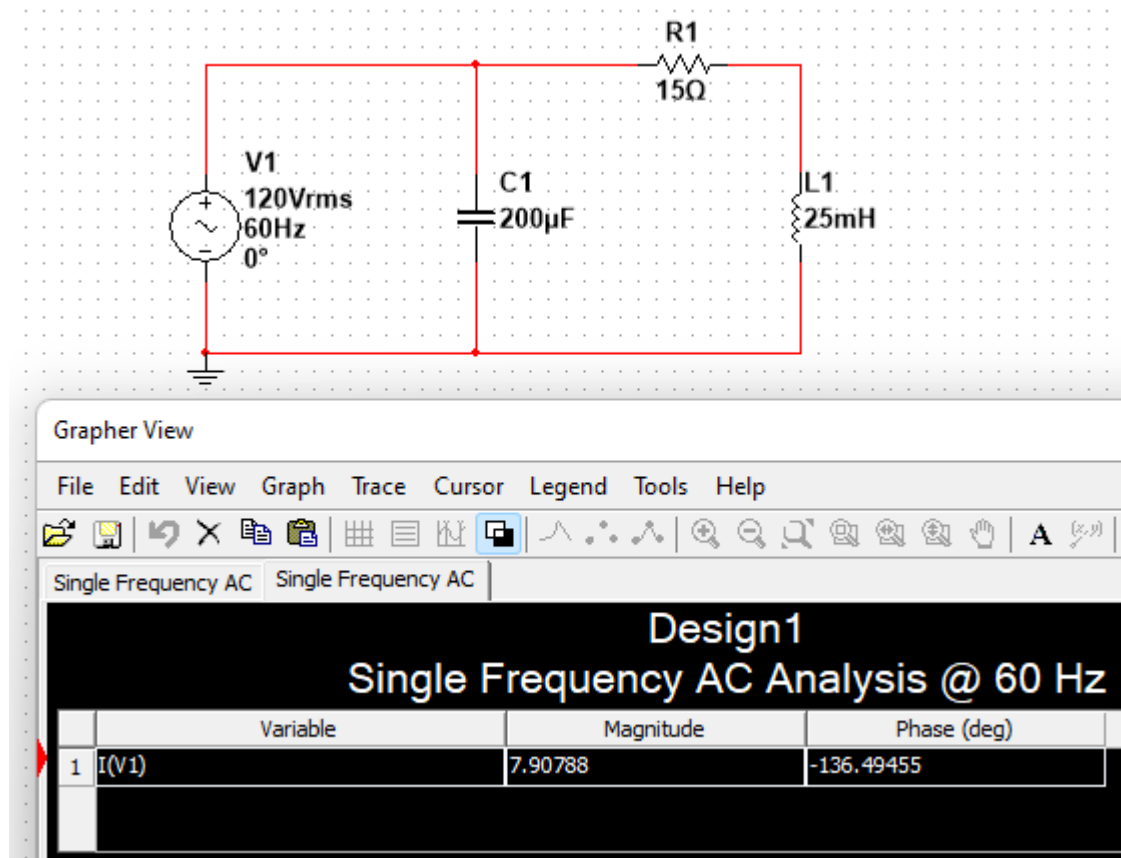

b) repetimos el ejercicio pero sin el capacitor

```
zeq = z1 + r;  
z_eq = [abs(zeq) angle(zeq)*gr] %angulo positivo = carga inductiva
```

```
z_eq = 1x2  
    17.715    32.142
```

```
i_f = vf/zeq;  
i_fasor = [abs(i_f) angle(i_f)*gr] %[A]
```

```
i_fasor = 1x2  
    6.7739   -32.142
```

```
S = abs(vf)*abs(i_f) %[VA]
```

```
S =  
812.86
```


```
fp = cos(angle(i_f)) %en atraso
```

```
fp =  
0.84673
```

```
P = S*fp %potencia activa consumida
```

```
P =  
688.28
```

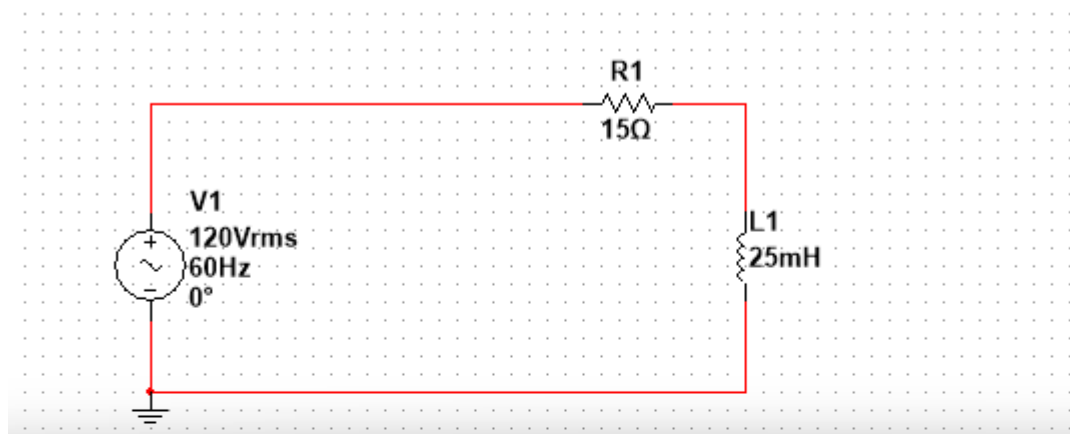En este caso vemos que el factor de potencia aumenta sin el capacitor, lo verificamos en el simulador:



Grapher View

Design1			
Single Frequency AC Analysis @ 60 Hz			
	Variable	Magnitude	Phase (deg)
1	I(V1)	6.77386	147.85809