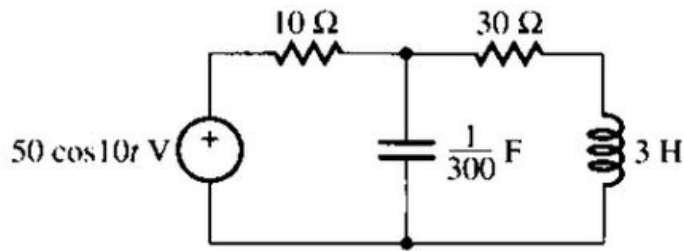


**12.21** (a) Find the real, reactive, and complex power delivered by the source in Figure P12.21. (b) What reactive element must be connected in parallel with the source to make its power factor 1?



**Figure P12.21**

primero convertimos todo a impedancias

```
clc, clear, close all
format short g

vf = 50;
w = 10;
f = w/(2*pi);
c = 1/300;
l = 3;

z1 = 10;
z2 = (1/(j*w*c));
z3 = 30;
z4 = j*w*l;
```

reducimos impedancias

```
zeq = 1/((1/(z3+z4))+(1/z2)) + z1 % impedancia equivalente[ohms] carga capacitiva
```

```
zeq =
    40 -    30i
```

```
If = vf/zeq % corriente [A]
```

```
If =
    0.8 +    0.6i
```

```
S = vf*conj(If)*0.5 % potencia compleja [VAR]
```

```
S =
    20 -    15i
```

Ahora calculamos el factor de potencia:

```
fp = cos(atan(imag(S)/real(S))) %en adelanto
```

```
fp =  
    0.8
```

como el factor de potencia esta en adelante sabemos que se conectará un elemento inductivo:

```
xp = ((real(zeq)^2)+(imag(zeq)^2))/(real(zeq)*tan(-acos(1))-imag(zeq))*j %
```

```
xp =  
    0 +    83.3331i
```

verificamos el nuevo factor de potencia:

```
lp = xp/(j*w) % inductancia en paralelo a la fuente
```

```
lp =  
    8.3333
```

```
zeq1 = 1/((1/zeq)+(1/(xp)))
```

```
zeq1 =  
    62.5
```

```
If = vf/zeq1
```

```
If =  
    0.8
```

```
S = vf*conj(If)
```

```
S =  
    40
```

```
fp = real(S)/abs(S)
```

```
fp =  
    1
```

Vemos que se ha corregido el factor de potencia, lo verificamos en el simulador:

